
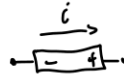


Rappel






$$q = 1.6022 \times 10^{-19} \text{ C}$$

$$v = \frac{dw}{dq}$$

$$i = \frac{dq}{dt}$$

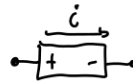


$$p = +i v \quad \text{ou} \quad -i v$$

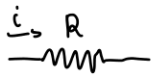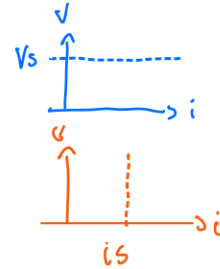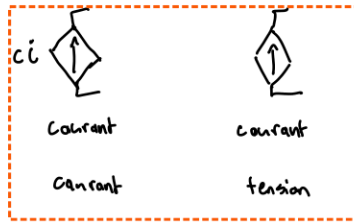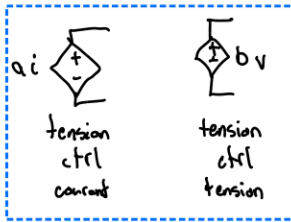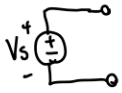

$$V = Ri$$

$$p = Ri^2 = \frac{V^2}{R}$$


$$G = 1/R$$

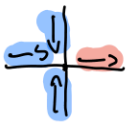


$$i_{in} = i_{out}$$



$$R = R_1 + R_2$$

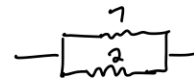
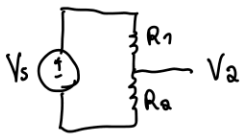
$$R = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$





$$V_2 = V_s \cdot \frac{R_2}{R_1 + R_2}$$



$$i_2 = i_s \cdot \frac{R_1}{R_1 + R_2}$$

Transphorm

$\Delta \quad Y$

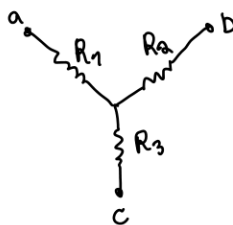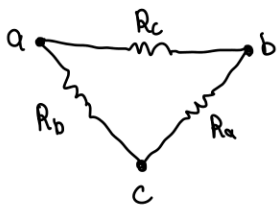

$$R_{ab} = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c} = R_1 + R_2$$

$$R_{ac} = \frac{R_b(R_a + R_c)}{R_a + R_b + R_c} = R_1 + R_3$$

$$R_{bc} = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c} = R_2 + R_3$$

$\Delta \rightarrow Y$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$Y \rightarrow \Delta$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$$